
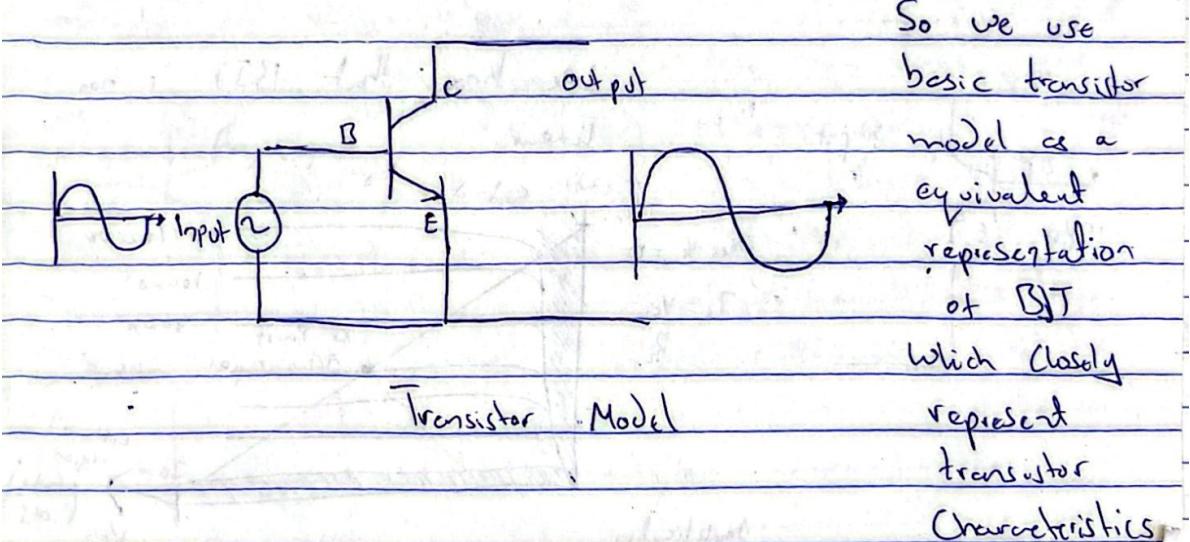


1

BJT Analysis

When we want to use a Transistor as an Amplifier we need to do 2 types of analysis

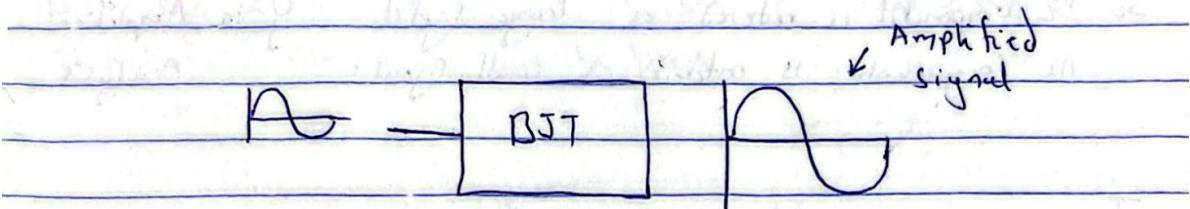- DC analysis - to find 1 Identify operating point
- AC analysis - to find gain and input and output impedances



Transistor Models

Based on the magnitude of the Input signal there are two transistor models

- Large Signal model
- Small Signal Model

(2)

When transistor is used as an Amplifier, then it
consist of 2 Components

Dc Components - Used for biasing the transistor


Ac Components - time varying signal, which we want to
amplify

So Dc component is referred as large signal in Amplifier

Ac components is referred as small signal Analysis

→ To understand behavior of the device for large signal
Large Signal model is used

We know that BJT is non

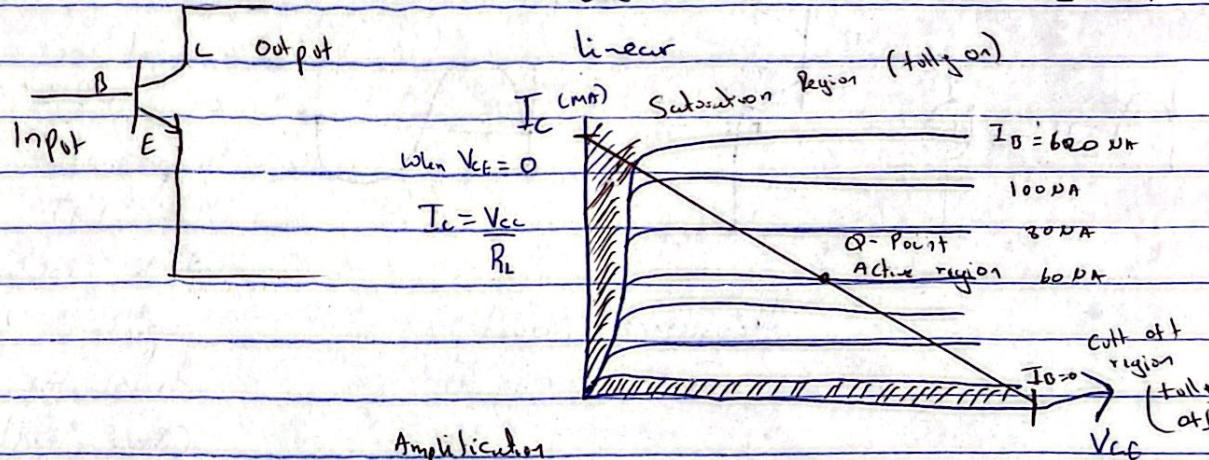


Active During We bias the When
 $\downarrow I_c = \beta I_B$ we operate in $I_c = 0$
When $V_{ce} = V_{cc}$


When the input signal is large the behavior of
signal is also non linear.

This is valid only when signal is operated in active
forward region.


Forward Active Region

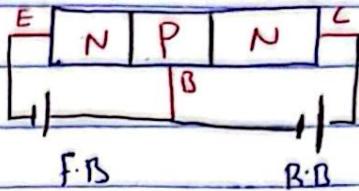

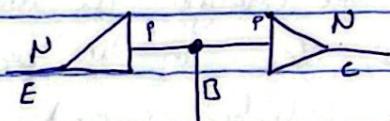
BJT has 2 PN junctions and it can be visualized as 2 transistors connected back to back



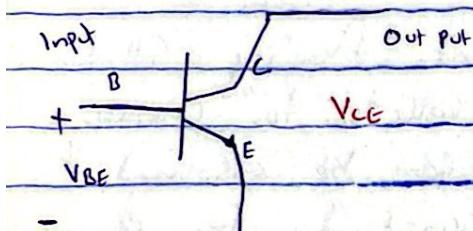In Common emitter configuration let's assume V_{CE} is constant and we are varying V_{BE}



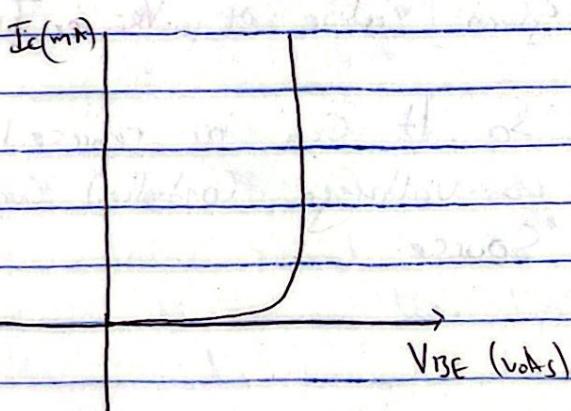Now by varying the Voltage V_{BE} + with load and measuring collector current I_C it will look similar to diode characteristic by drawing V_I Char




$$I_C = I_s \exp\left(\frac{V_{BE}}{V_T}\right) \rightarrow I_s \text{ is the relation b/w } V_{BE} \text{ and } I_C$$

I_s = Reverse Saturation current if its reverse biased

V_T = Thermal voltage

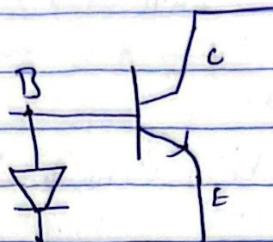(4)


From this curve we can say that the base emitter terminal can be replaced by (V_{BE}) by Diode




For common emitter Configuration
 I_C vs V_{CE} curve

for the fixed value of
 I_B or V_{BE}

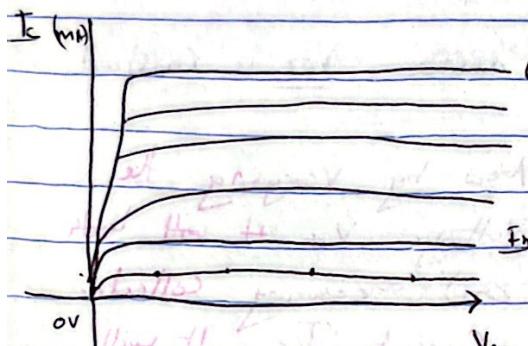If we change the voltage
 V_{CE} in the active region
the collector current almost
remains same (constant)



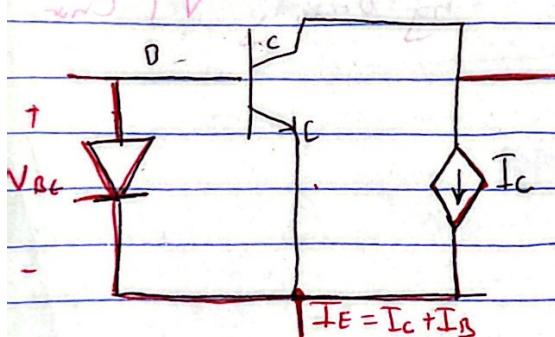→ The current flowing collector
to from collector to emitter
terminal can be assumed
to be constant for a
given value of V_{BE} or I_B



* So it can be represented
as voltage controlled current

Source.

And this is the equivalent representation of BJT
is the large signal model of BJT in forward active
region

$$I_B = \frac{I_S}{B} \exp\left(\frac{V_{BE}}{V_T}\right), \quad I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right)$$

$$I_c = \beta I_b$$


I_e = Summation of Collector Current and Base Current

$$I_e = (\beta + 1) I_b$$

$$\beta = \text{current gain} = \frac{I_c}{I_b}$$

$$I_c = (\beta + 1) \frac{I_s}{\beta} e^{\left(\frac{V_{BE}}{V_T}\right)}$$

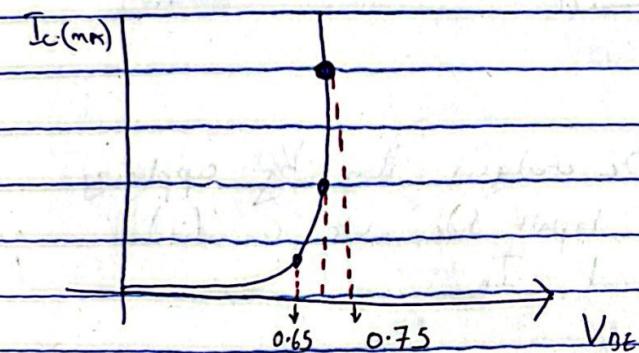The collector current depends upon V_{BE}
and the relationship is non linear




- even if the voltage V_{BE} changes by small amount.
- Then there is significant change in collector current

- If we do DC analysis of the circuit using the large signal model we always have to deal with this non linearity which will complicate the circuit so we never use non linear equations. So we approximate for the analysis

⑥

If we see I_c curve V_{BE} curve the variation in the voltage V_{BE} is very small.

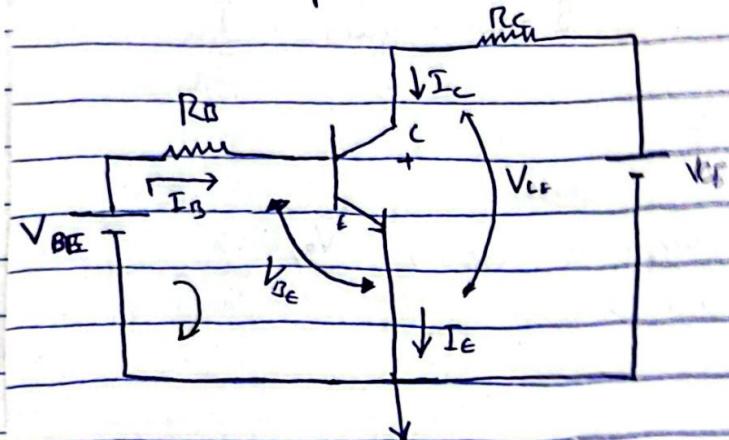So we approximate the value of V_{BE} as 0.7V



If we want to do DC analysis then by applying KVL equation on the input side we can find the value of base current I_B .

And then using equation $I_C = \beta I_B$

We can find the value of collector current I_C as well as the voltage V_{CE}

- This method gives the approximate value of the operating point.


If we want to find exactly values then we do Iterations

$$I_C = I_{S0} e^{\frac{V_{BE}}{V_T}}$$

$$V_{CE} = V_T \ln \left[\frac{I_C}{I_S} \right]$$

Small Signal analysis Model

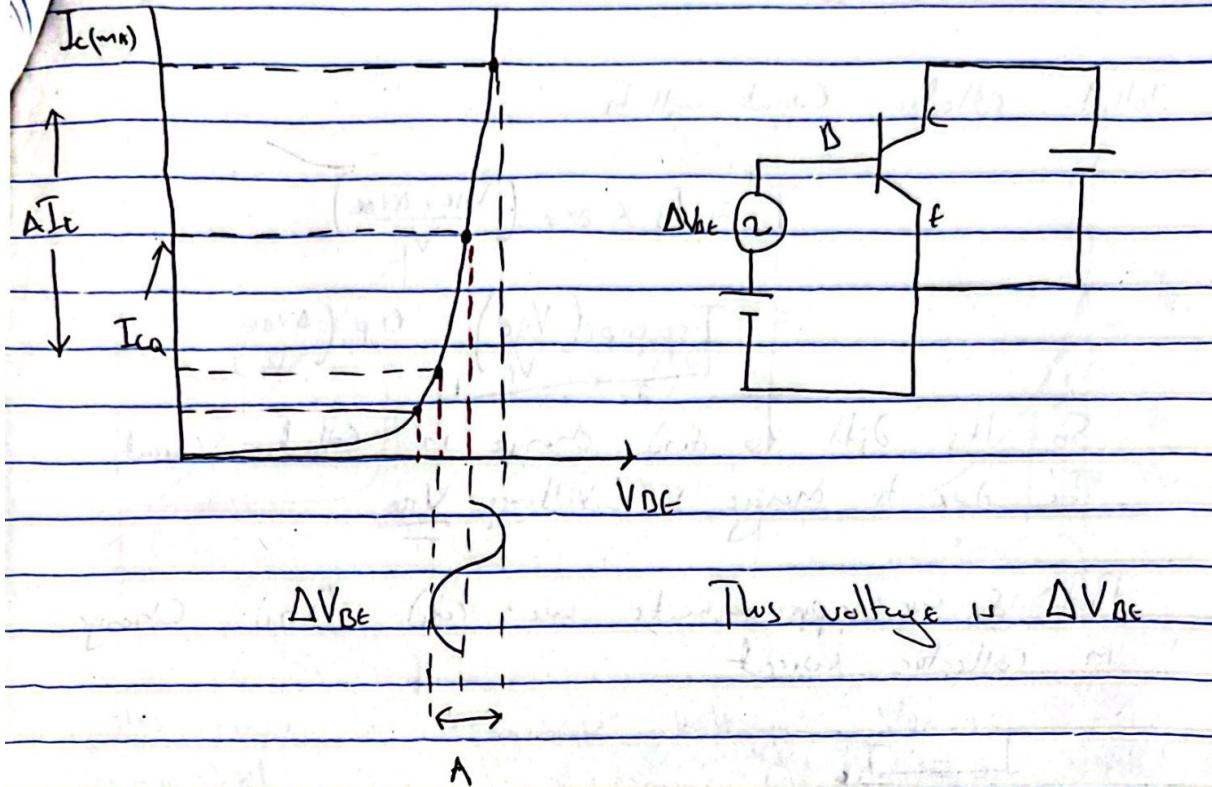We add a small ac signal in our DC signal analysis



Because of This small voltage there will be change in collector current

So this change in collector current to change in ΔV_{BE} is given as Trans-conductance

☞ measure how efficient a device such as transistor converts input voltage into output current

$$g_m = \frac{\Delta I_c}{\Delta V_{BE}} = A/V$$

→ The Small Signal is sinusoidal in nature

$$\Delta V_{ac} = V_m \sin \omega t$$

Total collector current will be

$$I'_c = I_s \times \exp \left(\frac{V_{be} + \Delta V_{be}}{V_T} \right)$$


$$= I_s \exp \left(\frac{V_{be}}{V_T} \right) \times \exp \left(\frac{\Delta V_{be}}{V_T} \right)$$

So it's diff to find change in collector current

I'_c due to change in voltage $\underline{V_{be}}$

But if we approximate we can find change in collector current

$$I'_c = I_c$$

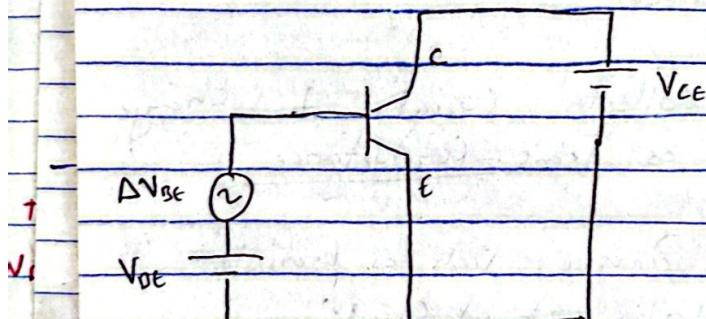


$$I'_c = I_c \times \exp \left(\frac{\Delta V_{be}}{V_T} \right)$$

Voltage ΔV_{be} = very small

When divide by $\frac{\Delta V_{be}}{V_T}$ is much less than one

$\ll 1$

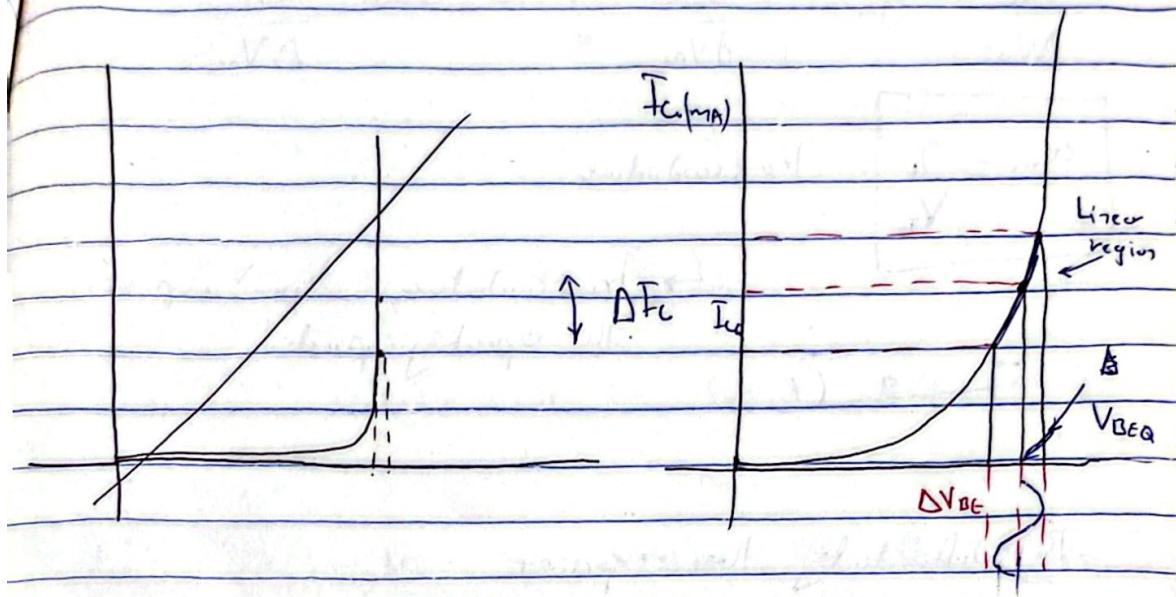if ΔV_{BE} is very small this means that we are operating on the linear region of the exponential curve



This means if change in voltage V_{BE} is sinusoidal, then the change in collector will also be sin sinusoidal

$$\text{and we can express as } I_c' = I_c \times \left(1 + \frac{\Delta V_{BE}}{V_T} \right)$$

$$e^{\frac{\Delta V_{BE}}{V_T}} = 1 + \frac{\Delta V_{BE}}{V_T}$$

for small value, \approx

$$e^x \approx 1 + x + \frac{x^2}{2!} \dots$$

(approx)

we can say $1 + x$

$$I_c' = I_c + I_c \frac{\Delta V_{BE}}{V_T}$$

$\Delta I_c \leftarrow$ This is

10

$$\Delta I_c = \frac{I_c \times \Delta V_{BE}}{V_T} = \frac{\Delta I_c}{\Delta V_{BE}} = \frac{I_c}{V_T}$$

↓
as we discuss)

$$\frac{\Delta I_c}{\Delta V_{BE}} = g_m = \frac{d(I_c)}{dV_{BE}} \rightarrow \text{for small } \Delta I_c$$

$$g_m = \frac{I_c}{V_T}$$

Transconductance

→ Transconductance depend upon
the operating point

$$I_c + g_m (1)$$

By differentiating this expression

$$I_c = I_s \exp\left(\frac{V_{BE}}{V_T}\right)$$

$$\frac{dI_c}{dV_{BE}} = I_s \exp\left(\frac{V_{BE}}{V_T}\right) \times \frac{1}{V_T}$$


$$g_m = \frac{I_c}{V_T}$$

Transconductance expression

This depends on operating point as the
value of I_c increases the transconductance will also
increase

If $I_c \uparrow$ for the same change in base-emitter
voltage there will be more change in collector
current.
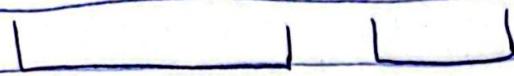
$$I_s \times e^{\left(\frac{V_{ne}}{V_t} \right)} + g_m \Delta V_{ne}$$





Dc biasing voltage ΔI_c
 V_{BE}

Collector current - Small change \rightarrow Signal I_c
 Large model

So we can separate the signals


- During DC analysis we can consider all AC sources to zero

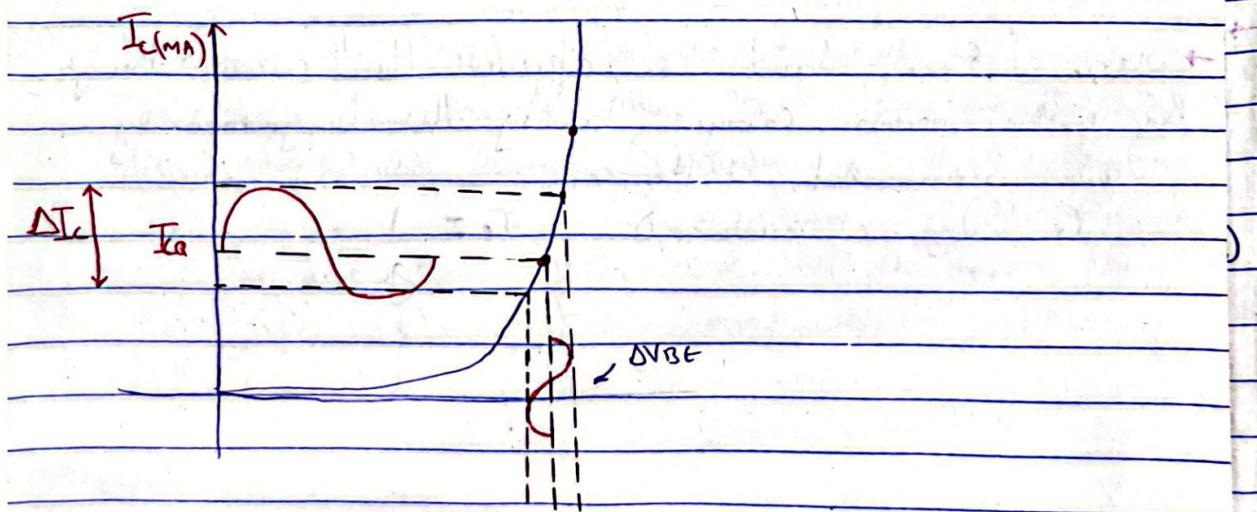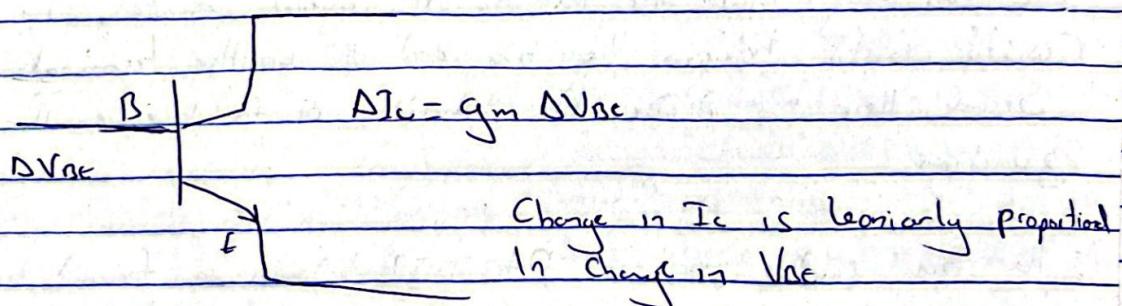During AC analysis we consider all DC source to zero



12

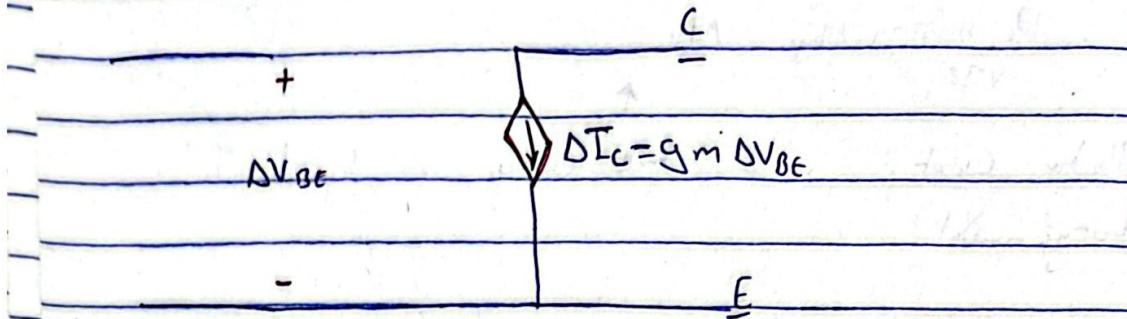So In Small Signal model we can represent
as Voltage Controlled Source Current Source.



When there is change in I_c there is also change
in Base current I_B

$$\Delta I_B = \frac{\Delta I_c}{\beta} = \frac{g_m}{\beta} \Delta V_{BE}$$



This relationship is linear

→ We can say that in the Small-Signal model, the resistor exists between the base and the emitter terminal.
because there is diode like behavior at the base-emitter junction

- The base-emitter junction of BJT behaves as forward biased diode during operation

→ When a small signal is applied the current through
Base-emitter junction changes slightly this is governed by
Diode incremental resistance
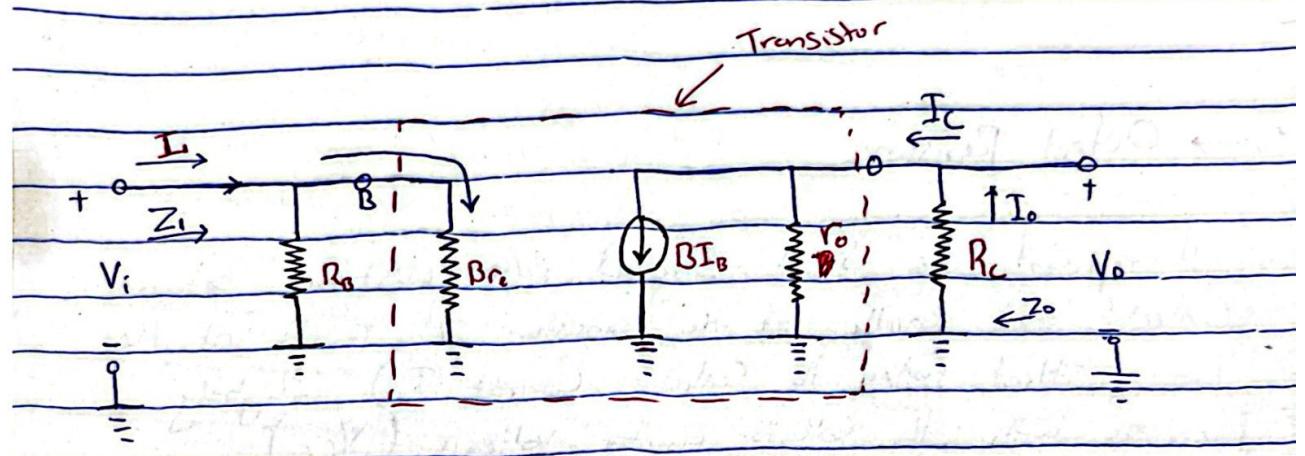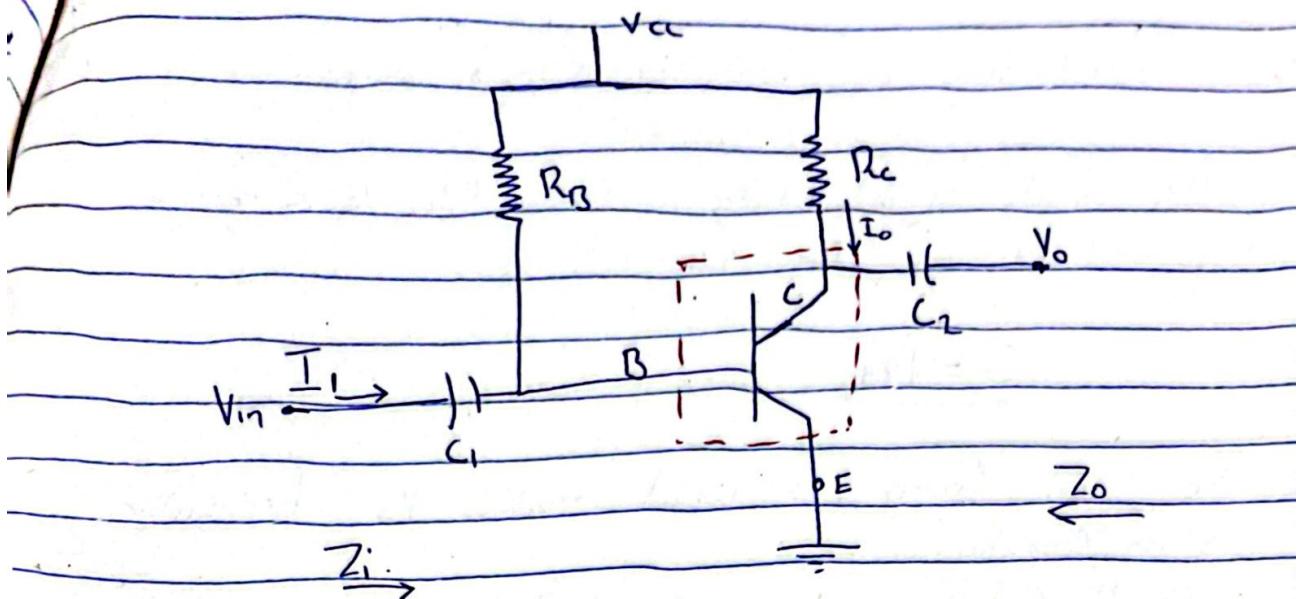
$$r_e \text{ (dynamic resistance)} \quad r_e = \frac{1}{g_m}$$



Bre :- Base-emitter resistance b/w base and emitter of a transistor. It models the fact that base-emitter junction behaves like forward-biased diode

- It affects the Input Impedance of transistor
- The higher Bre increases the Input Impedance, which is desired for Input Signal Sensitivity
- It determines how much Input Voltage (V_i) is needed to drive certain base current (I_B)

$\text{BI}_0 \rightarrow$ Current Gain and Controlled Current Source

- The Small-Signal Collector Current (\bar{I}_c) is Directly proportional to base current (\bar{I}_B)

$$\bar{I}_c = \beta \bar{I}_B$$

The Current Source is what makes the transistor CS or Amplifier.

- As It Controls a Large Current (I_c) using Small Current (I_B)

$r_o \rightarrow$ Output Resistance

- It represents the Small Signal O/P resistance between Collector and Emitter of the Transistor. It results from the Early effect, when the Collector Current (I_c) slightly increases with the Collector-Emitter Voltage (V_{CE})

- r_o models the non-ideal behavior of the Transistor
- In ideal Transistor, r_o would be infinite \rightarrow meaning the Output Current (I_c) would be independent of (V_{CE})

→ → The Small-Signal equivalent circuit incorporates

1) Input Side:- The Input Voltage (V_i) applied across ~~Bre~~ Bre which determines the base current (\bar{I}_B)

2) Amplification:- The Transistor amplifies the Base Current (\bar{I}_B) into collector current (I_c) $\bar{I}_c = (\beta \bar{I}_B)$ using Controlled Current Source ($\beta \bar{I}_B$)

Output Side:- The amplified current (i_o) flows through the O/p resistance (r_o) and load resistance (R_L), determining the o/p voltage (V_o .)