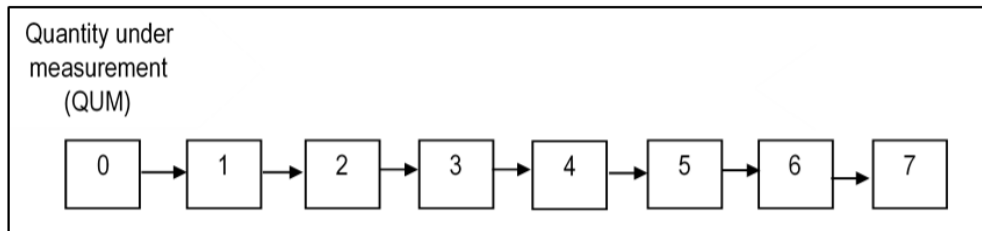


## INSTRUMENTATION AND MEASUREMENTS


### SELF ASSESSMENT QUESTIONS

BEng23 CoE

1. Figure below is a generalized block diagram of a measurement system that contains the following components: Quantity under measurement (QUM), amplifier, sensor, digital signal processor (DSP), anti-aliasing filter, analogue-to-digital inverter (ADC), signal conditioning filter, and data representation.
  - a) Match the block number with the name of the component.  
Example: 0 - Quantity under measurement (QUM)
  - b) Mention the block (shown in Figure ) which is responsible for the following noise sources:
    - i)  $n_1$  = noise accompanying the QUM
    - ii)  $n_2$  = equivalent noise from electronics
    - iii)  $n_3$  = equivalent quantization noise.



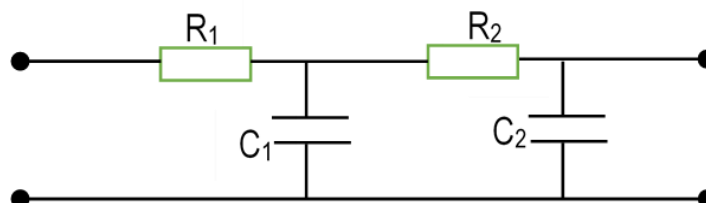
2. Resistance  $R_X$  is measured by using voltmeter of  $1000\ \Omega$  resistance and a milliammeter of  $0.8\ \Omega$  resistance by voltmeter– ammeter method. If the voltmeter reads 12 V and milliammeter reads 62 mA, calculate the percentage error in the values of measured resistances if:
  - a) The method case 1 is as shown in the figure above
  - b) The method case 2, is as shown in Figure above
  - c) Which method among the two is the appropriate?
3. Figure below is a second order passive low pass filter. Obtain the following:
  - a) Transfer function
  - b) Natural frequency,  $f_n$  .
  - c) If  $R_1 = 10\ \text{k}\Omega$ ,  $R_2 = 40\ \text{k}\Omega$ ,  $C_1 = 0.1\ \mu\text{F}$ , and  $C_2 = 0.1\ \mu\text{F}$ , calculate the natural frequency,




Note that, for the standard second order system:

$$G(s) = \frac{\omega_n^2}{s^2 + 2\xi\omega_n s + \omega_n^2}, \text{ and } f_c = f_n \sqrt{1 - 2\xi^2 + (4\xi^4 - 4\xi^2 + 2)^{\frac{1}{4}}}$$

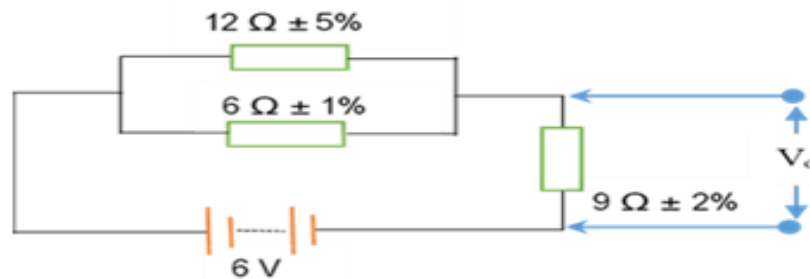4. List down four major applications of the ac potentiometers
  - a) A single-range laboratory-type potentiometer has 20 steps dial switch where each step represents 0.1 volt. The dial resistors are  $10\ \Omega$  each. The slide wire of the potentiometer is circular and has 10 turns and a resistance of  $1\ \Omega$  per turn. The slide wire has 100 divisions and interpolation can be done to one fifth of a division. The working battery has a voltage of 12.0 volt. Calculate
    - (i) the measuring range of the potentiometer
    - (ii) the resolution
    - (iii) working current,
    - (iv) setting of the rheostat.
5. From Figure below, the voltage, current and dissipated power across the  $9\ \Omega \pm 2\%$  resistor are to be measured using voltmeter and ammeter only.



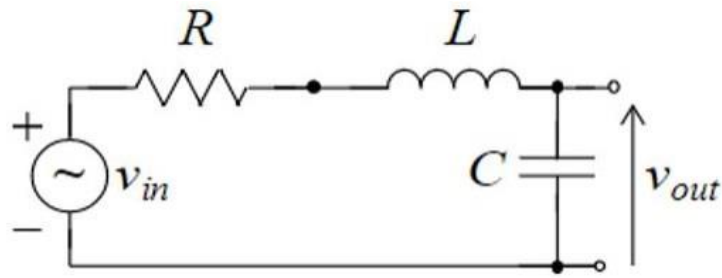- a) Obtain the maximum percentage error of the measured voltage, current, and power, assume that:
    - i. The measuring instruments are error free.
    - ii. The accuracy of measuring instruments are as follows: voltmeter ( $\pm 0.1\%$ ), ammeter ( $\pm 0.1\%$ ), and power is obtained by using the formula  $V \times I$ .
  - b) If the equivalent resistor is to be replaced, state the overall:
    - i. Absolute error.
    - ii. Relative error
    - iii. Tolerance
6. From the given circuit shown in Figure below, if  $L = 0.1\ \text{mH}$ ,  $C = 1\ \mu\text{F}$ , and  $R = 10\ \Omega$ , find the value of the following three parameters:



- a) static sensitivity,
- b) natural frequency, and
- c) damping ratio.

where, the normalized (dimensionless) transfer function,  $G(s)$  is given as

$$G(s) = \frac{K}{s^2 + 2\xi\omega_n s + \omega_n^2}$$

7. **A.** With an aid of block diagram, list and explain the elements of a data acquisition system.
- B.** An 8-bit ADC is used to convert a temperature signal which has a measuring range of 0 deg C to 800 deg C. find the following
- a) Number of quantization levels and the resolution of the temperature of an ADC
  - b) Quantization level when the temperature is 512 deg C
  - c) Determine the quantization error when the temperature input is 512 deg C.