

Experiment (2): OP-AMP AUDIO AMPLIFIER

• Objectives

- To measure the open-circuit voltage gain, loaded voltage gain, input resistance, and output resistance of the common emitter amplifier.
- To evaluate the common emitter amplifier using the small-signal equivalent model.
- To demonstrate the differences in voltage gain and input resistance due to the removal of the emitter bypass capacitor.

• Procedure

- Identify the op-amp configuration
- Applying the signal generator's frequency set to 300 Hz, $V_s = 50\text{mVp-p}$ and the supply voltage of +15 Vcc and -15 VEE in figure 2.1;
- Calculate the maximum and minimum voltage gains of the op-amp.
- What is the maximum rms output of the op-amp stage if the input is 50 mVrms?
- Determine the ideal maximum power delivered by the audio amplifier to an
- Speaker
- From the scope display , determine the rms value of each voltage.
- Determine the voltage gain of the op-amp stage from the measured signals.
- Determine the overall voltage gain from the measured signals.

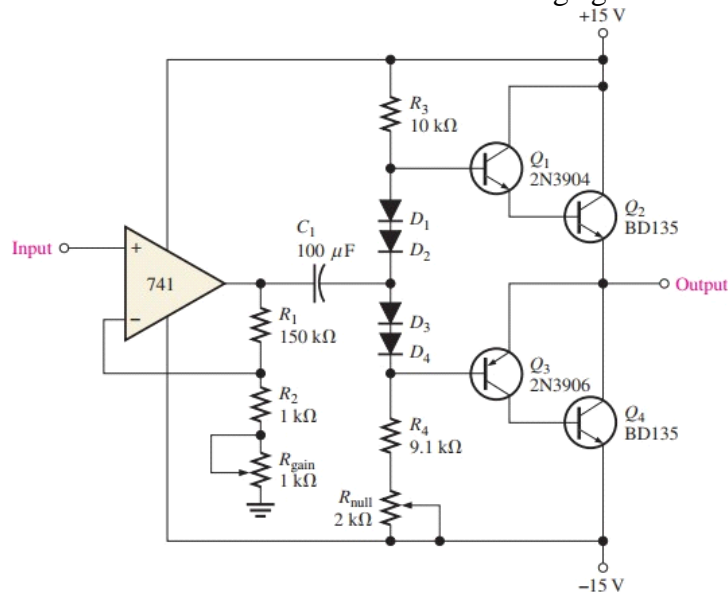


Figure 2.1

