


TWO-PORT CIRCUITS

CONTENTS

- 1 Definition of Two-Port Circuits
- 2 Classification of Two-Port Parameters
- 3 Finding Two-Port Parameters
- 4 Analysis of the Terminated Two-Port Circuit
- 5 Interconnected Two-Port Circuits

Definition of Two-Port Circuits

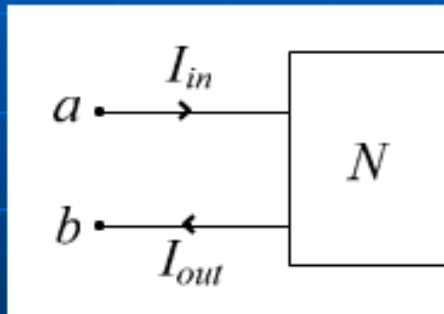
Consider a linear two-terminal circuit N consisting of no independent sources as follows :



For a, b two terminals,
if $I_{in} = I_{out}$, then it
constitutes a port.

Definition of Two-Port Circuits

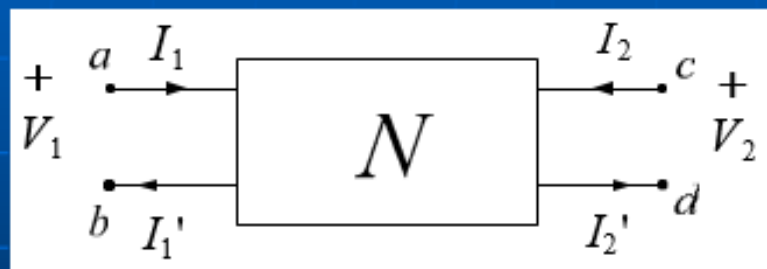Now consider the following linear four-terminal circuit containing no independent sources.




with $I_1 = I_1'$

$I_2 = I_2'$

Then terminals a, b constitute the input port and terminals c, d constitute the output port.

Definition of Two-Port Circuits

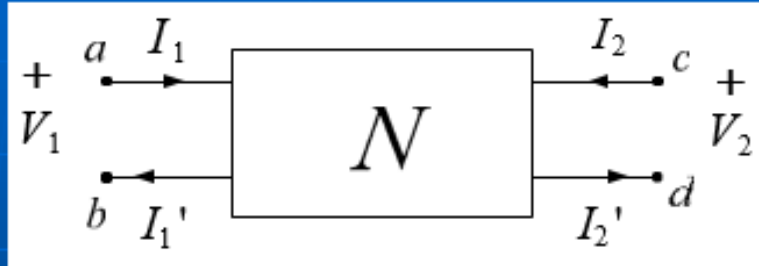

No external connections exist between the input and output ports.

The **two-port model** is used to describe the performance of a circuit in terms of the voltage and current at its input and output ports.

Purpose of the two-port model

- A **two-port network** (four-terminals network) is an electrical network (circuit) or device with two *pairs* of terminals to connect to external circuits.
- Two terminals constitute a port if the currents applied to them satisfy the port condition:
 - ❑ the electric current entering one terminal must equal to the current emerging from the other terminal on the same port.
- The ports constitute interfaces where:
 - ❑ the network connects to other networks,
 - ❑ the points where signals are applied or outputs are taken.
- In a two-port network, often port 1 is considered the input port and port 2 is considered the output port.

- The two-port network model is used in mathematical circuit analysis techniques to isolate portions of larger circuits.
- A two-port network is regarded as a "**black box**" with its properties specified by a matrix of numbers.
- **Advantages;** Response calculation, Comparing circuits
 - ❑ The response of the network to signals applied to the ports can be calculated easily, without solving for all the internal voltages and currents in the network.
 - ❑ It also allows similar circuits or devices to be compared easily.
- Any linear circuit with four terminals can be regarded as a two-port network provided that it does not contain an independent source and satisfies the port conditions.

- Examples of circuits analyzed as two-ports are filters, matching networks, transmission lines, transformers, and small-signal models for transistors (such as the hybrid-pi model).
- In two-port mathematical models, the network is described by a 2 by 2 square matrix of complex numbers.
- The common models that are used are referred to as *z-parameters*, *y-parameters*, *h-parameters*, *g-parameters*, and *ABCD-parameters*.
- These are usually expressed in matrix notation, and they establish relations between the variables
 - ❑ V_1 = voltage across port 1
 - ❑ I_1 = current into port 1
 - ❑ V_2 = voltage across port 2
 - ❑ I_2 = current into port 2

Definition of Two-Port Circuits

Two-port circuits are **useful in** communications, control systems, power systems, and electronic systems.

They are also useful for **facilitating cascaded design** of more complex systems.

Classification of Two-Port Parameters


There are **four terminal variables**, namely V_1, V_2, I_1, I_2 , only two of them are independent.

Hence, there are **only six possible sets of two-port parameters**.

$${}^4C_2 = \frac{4 \times 3}{2 \times 1} = 6$$

Classification of Two-Port Parameters

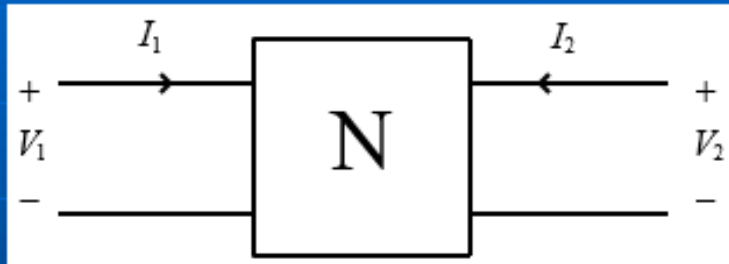(1) The impedance, or Z, parameters Z Parameters




$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}, Z_{ij} \text{ in } \Omega$$

For two-port networks, four parameters are generally required to represent the circuit.

Classification of Two-Port Parameters

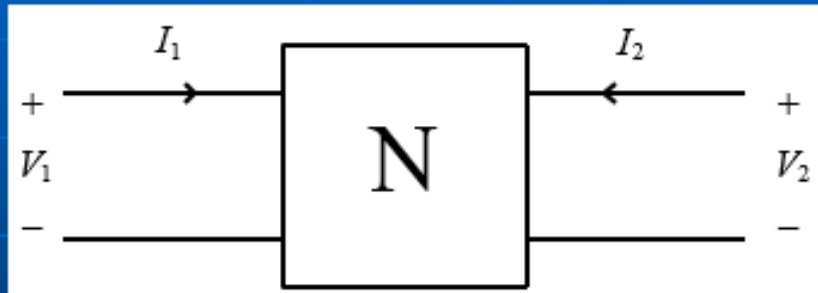
(2) The admittance, or Y , parameters Y Parameters



$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}, \quad Y_{ij} \text{ in } S$$

Classification of Two-Port Parameters

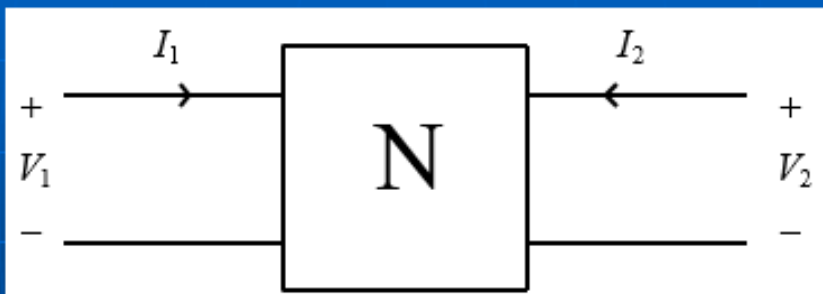(3) The hybrid , or h , parameters H Parameters



$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}, \quad \begin{array}{l} h_{11} : \text{in } \Omega \\ h_{22} : \text{in } S \\ h_{12} \text{ \& } h_{21} : \text{scalars} \end{array}$$

Finding Two-Port Parameters

Method 1: Calculate or measure by invoking appropriate short-circuit and open-circuit conditions at the input and output ports.

Method 2: Derive the parameters from another set of two-port parameters.


Open-circuit the Port 1
Short-cct Output

Finding Two-Port Parameters

Method 1 : Choose Z parameters as an illustration.

$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$

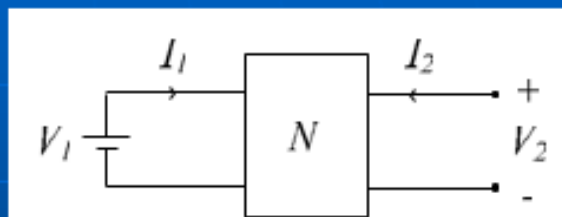


when $I_2 = 0$, output port is open

$$V_1 = z_{11}I_1, \therefore z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad , \text{input impedance}$$

$$V_2 = z_{21}I_1, \therefore z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} \quad , \text{transfer impedance}$$

Finding Two-Port Parameters

When $I_1 = 0$, input port is open

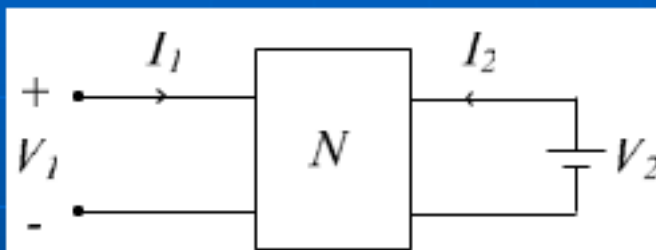

$$V_1 = Z_{12} I_2 \quad Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}, \text{ transfer impedance}$$

$$V_2 = Z_{22} I_2 \quad Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}, \text{ output impedance}$$

When the two-port does not contain any dependent source, then $Z_{12} = Z_{21}$.

Finding Two-Port Parameters

z_{11} & z_{22} are called **driving-point impedances**.


z_{12} & z_{21} are called **transfer impedances**.

When $z_{11}=z_{22}$, the two-port circuit is said to be symmetrical.

When $z_{12}=z_{21}$, the two-port circuit is called a **reciprocal circuit**.

Finding Two-Port Parameters

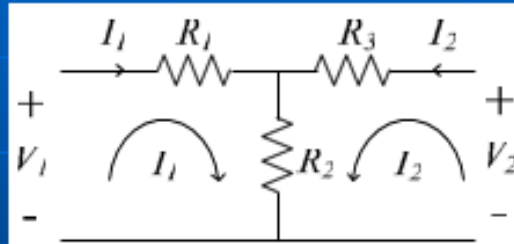Example 1 : Find the Z parameters of the T-network




Assign mesh currents
as shown :

$$\begin{bmatrix} R_1 + R_2 & R_2 \\ R_2 & R_2 + R_3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\therefore z_{11} = R_1 + R_2$$

$$z_{12} = z_{21} = R_2$$


$$z_{22} = R_2 + R_3$$

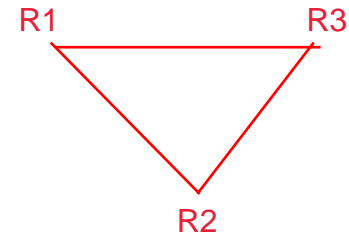

Finding Two-Port Parameters

A two-port can be replaced by the following
equivalent circuit.

Equivalent Circuit

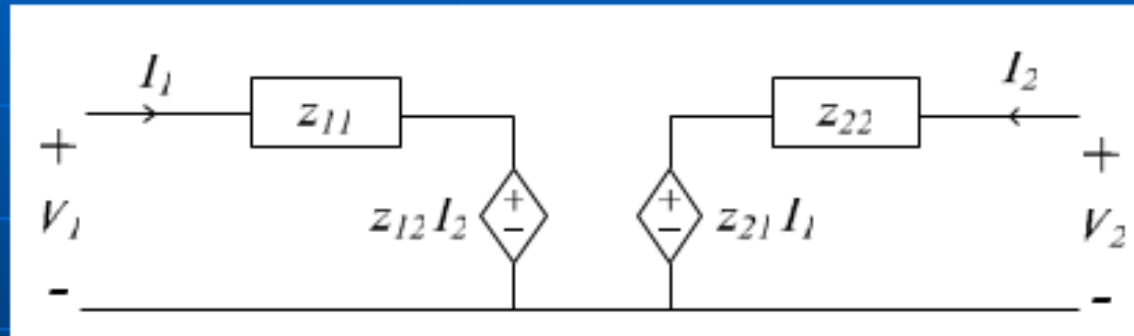


$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$


Finding Two-Port Parameters

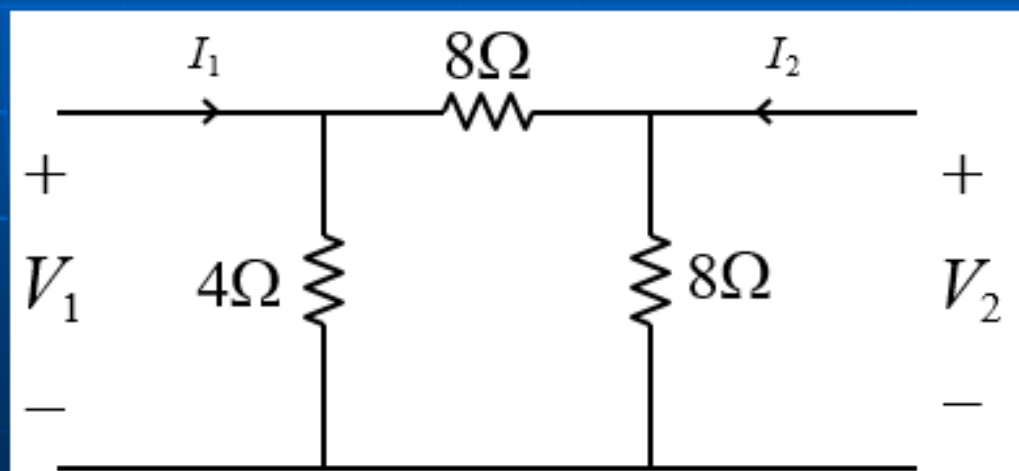Example 2: Find the Z parameters of the following circuit by definition of Z parameters.



Finding Two-Port Parameters

Step 1: Let $I_2 = 0$ and apply V_1

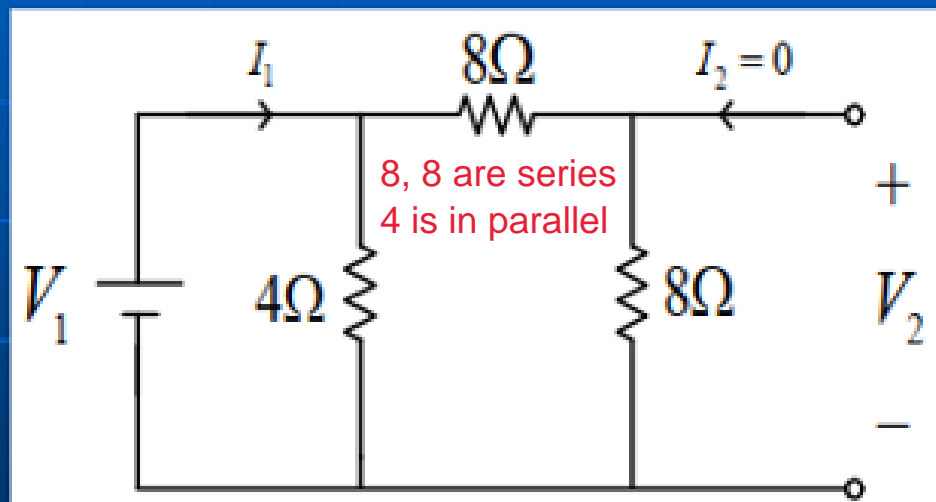

$$I_1 = V_1 / (4\Omega // (8 + 8)\Omega) = \frac{20}{64} V_1$$


$$V_2 = \frac{8}{8 + 8} V_1 = \frac{1}{2} V_1$$

$$\therefore z_{11} = \frac{V_1}{I_1} = \frac{64}{20} = \frac{16}{5} \Omega$$

$$z_{21} = \frac{V_2}{I_1} = \frac{\frac{1}{2} V_1}{I_1} = \frac{1}{2} z_{11} = \frac{8}{5} \Omega$$

Finding Two-Port Parameters

Step2: Let $I_1 = 0$ and apply V_2

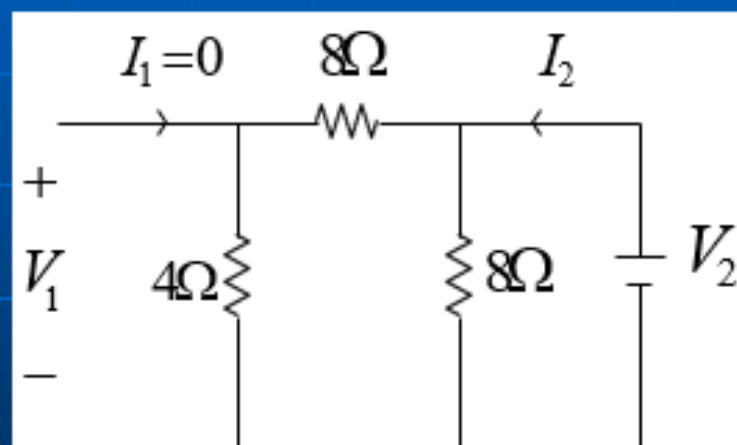

$$I_2 = V_2 / (8\Omega // (8 + 4)\Omega) = \frac{5}{24}V_2$$

$$V_1 = \frac{4}{4 + 8}V_2 = \frac{1}{3}V_2$$

$$\therefore z_{22} = \frac{V_2}{I_2} = \frac{24}{5}\Omega$$

$$z_{12} = \frac{V_1}{I_2} = \frac{\frac{1}{3}V_2}{\frac{5}{24}V_2} = \frac{1}{3}z_{22} = \frac{8}{5}\Omega$$

$$\therefore [Z] = \begin{bmatrix} 16/5 & 8/5 \\ 8/5 & 24/5 \end{bmatrix} \Omega$$

Determine the Z parameter matrix of the port networks below



Homework: If the Z-parameters for the T-network as shown below are $Z_{11} = 40\Omega$, $Z_{22} = 50\Omega$ and $Z_{12} = Z_{21} = 30\Omega$, then what are the values of Z_1 , Z_2 and Z_3 ?



$$Z_{11} = Z_1 + Z_3$$

$$Z_{12} = Z_{21} = Z_3$$

$$Z_{22} = Z_3 + Z_2$$

$$Z_3 = Z_{12} = Z_{21} = 30 \text{ ohms}$$

$$Z_2 = Z_{22} - Z_3 = 50 - 30 = 20 \text{ ohms}$$

$$Z_1 = Z_{11} - Z_3 = 40 - 30 = 10 \text{ ohms}$$

- a) 10 ohm, 20 and 30
- b) 20 ohm, 30 and 20
- c) 30 ohm, 40 and 10
- d) 40 ohm, 50 and 10